

Term End Examination - May 2013

Course : ITE205 - Digital Electronics and Microprocessors Slot: G2+TG2

Class NBR : 3982

Time : Three Hours Max.Marks:100

Answer ALL Questions a) Using 10's complement perform following subtraction 1. [4] 72532 - 3250 b) Solution to the quadratic equation $X^2-10X+31=0$ is X=5, X=8. What is the base of [4] the numbers c) Perform the following conversion [2] 11001.11102 = (?)10a) Find the complement of F = x+yz and then show that FF' = 0 and F+F' = 1. 2. [5] b) Design gray to binary decoder and convert the following gray codes into binary [5] codes (i)10101 (ii)110101 i) What is Full adder and how it is different from half adder? Implement Full-adder 3.(a)[5] using half adders. ii) Implement the Boolean function $F(x,y,z) = \sum (1,2,6,7)$ using 4 x 1 mux. [5] OR a) Explain the working of carry look ahead adder with a neat sketch 3.(b)[5] b) Implement the following functions using decoder [5] (i) f(A,B,C) = A+BC(ii) f(A,B,C) = B + C4. Design 4-bit binary synchronous counter using 'D' Flip-flops. [10]

5.(a)	What is race around problem and explain the three possible solutions to eliminate it?	[10]
	OR	
5.(b)	A digital system has a clock generator that produces pulses at a frequency of 80MHz.Design a circuit that provides a clock with a cycle time of 50ns using (i)'D' flip-flop (ii) J K Flip-flop	[10]
6.	Explain the operation of dual slope ADC. Write the advantages and disadvantages of dual slope ADC compared to successive approximation.	[10]
7.	What is meant by addressing mode? Explain all the addressing modes of 8086 microprocessor with suitable examples.	[10]
8.	Briefly explain the maximum mode of 8086 mocroprocessor and draw the memory read and write timing diagram in maximum mode.	[10]
9.	Draw the block diagram of DMA controller and explain the operation of it.	[10]
10.	a) Design XOR gate using 2X1 MUX	[2]
	b) Design 2-bit synchronous binary down counter with J K Flip-flops.	[2]
	c) Draw the block diagram of ladder type DAC	[2]
	d) What are the different flags in 8086?	[2]
	e) Explain shortly about USART.	[2]

 $\Leftrightarrow \Leftrightarrow \Leftrightarrow$